

| Raspberry Pi. We learned how to make connections with GPIO pins and control the LED. Lets go one step further and write program to detect motion and send the notifiction on telegram channel. |
|--|
| |
| |
| In this article we will cover below things: |
| - Printing message on terminal when motion is detected |
| - Connecting PIR motion detection sensor, buzzer and LED to GPIO pins |
| - Activating the buzzer and LED on motion detection |
| |
| |
| |
| We are using Raspberry Pi 3 B+ model. |
| |
| |
| Requirements: |
| |
| We will require below components (apart from Raspberry Pi obviously :D) to make this work. |
| |
| - Breadboard |
| - Jumper Wires |
| - Buzzer (Optional) |
| - LED |
| - Resistors |
| - PIR motion detection sensor |
| |

| Printing message on terminal when motion is detected: |
|--|
| Here we will print a simple message 'motion detected' on the screen when motion is detected by PIR motion detection sensor. To know more about working of PIR motion detection sensor please refer this wikipedia article. |
| Connections: |
| PIR motion detection sensor have three pins. If you remove the plastic cover from the PIR sensor, you will be able to see which pin needs to be connected to where. Refer the picture below. |
| pir motion sensor |
| Left pin needs to be connected to 5v pin, middle pin will be send the output when motion is detected and right pin will be connected to ground pin. |
| So we connect the left pin to 2nd pin of GPIO set on Raspberry Pi. Middle one to any pin which can be set to receive the output, 11 in our case and right pin to 6th pin. See the image with connections below. |

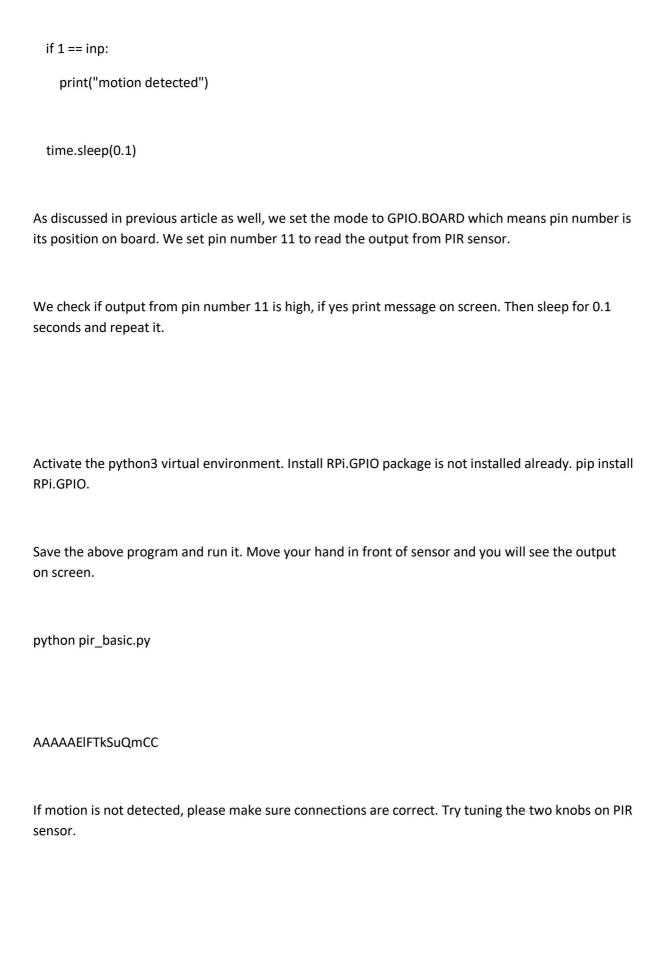

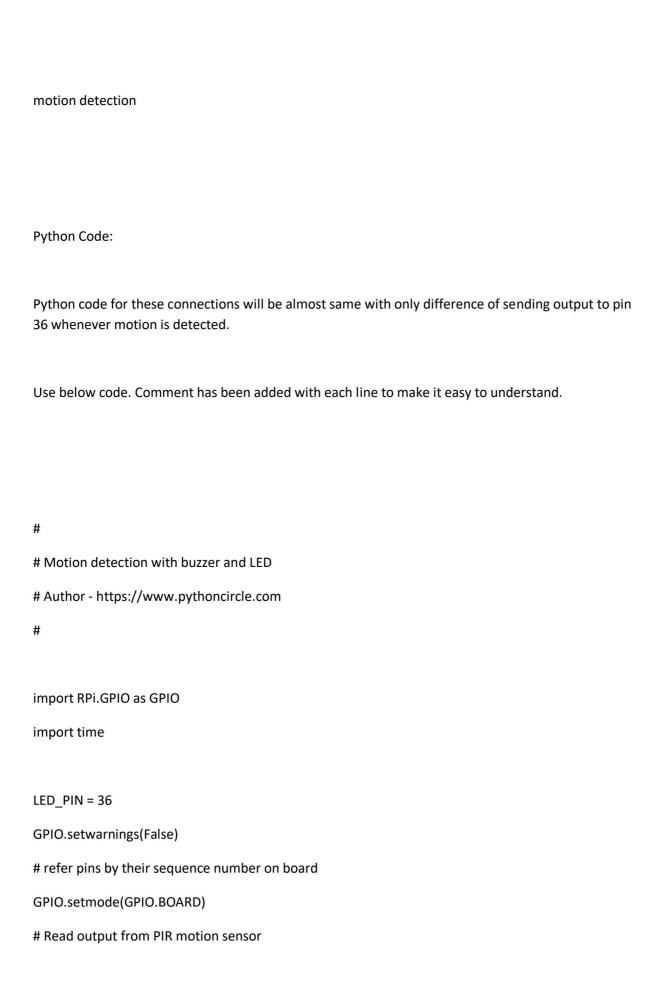

| Connecting Buzzer and LED: |
|---|
| This time when motion is detected we will activate a buzzer and turn on the LED. |
| This is the first time we will be connecting more than one component on breadboard. Please follow below instructions to make connections. |
| - Connect pin 2 (5v) to live column of breadboard. |
| - Connect pin 6 (ground) to ground column of breadboard. |
| - Connect left pin (5v) of PIR sensor to live column of breadboard. |
| - Connect middle pin (output) to pin 11 of GPIO pin set of Raspberry Pi. |
| - Connect right pin (ground) to ground column of breadboard. |
| - Connection of PIR sensor is done using breadboard. Now lets connect the LED and buzzer. |
| - Connect the positive end of LED (longer leg) to pin 36 but with 220 ohm resistor in between. Refer previous article. |
| - Connect the neutral end of LED (smaller leg) to ground column on breadboard. |
| - Connect the Positive terminal of buzzer to pin 36. Connect negative terminal to ground column of breadboard. |
| Refer below diagram and picture for connections. |
| pir motion sensor connections |



```
GPIO.setup(11, GPIO.IN)
# LED output pin
GPIO.setup(LED_PIN, GPIO.OUT)
while True:
 i = GPIO.input(11)
 # When output from motion sensor is LOW
  if i == 0:
    print("No motion")
    # Turn OFF LED and buzzer
    GPIO.output(LED_PIN, 0)
  # When output from motion sensor is HIGH
  elif i == 1:
    print("motion detected")
    # Turn ON LED and buzzer
    GPIO.output(LED_PIN, 1)
  time.sleep(0.1)
```

When you run the above code and motion is detected, LED is turned on and buzzer is activated.

If something is not working for you, feel free to comment.